

Time: 2½ hrs.

Note:

1. All questions are compulsory with internal choice.
2. Draw neat diagrams wherever necessary.
3. Figures to the right indicate full marks.

Marks:75

Q.1 Answer the following (any three)

(15)

(a) Convert :

i. $(125)_{10}$ to $(?)_2$

ii. $(127)_8$ to $(?)_2$

(b) Solve using 1's complement.

i) $12 - 10$ ii) $12 - 13$

(c) Multiply :

i) $(1101) \times (101)$

ii) $(1110) \times (110)$

(d) Convert in to BCD :

i) $(256)_{10}$

ii) $(512)_{10}$

(e) Perform :

i) $(1101011) + (101010)$

ii) $(1101011) - (101011)$

(f) Explain Basic gates with symbol and truth table.

Q.2 Answer the following (any three)

(15)

(a) Explain Demorgan's laws.

(b) Describe NOR and XOR gate with Symbol, Truth table, Boolean expression and Waveform.

(c) Draw the circuit diagram for following Boolean expression.

i. $\bar{A}B + \bar{A}\bar{B}$

ii. $\bar{A} + BC + \overline{(BC)}$

(d) Explain with the help of circuit diagram how NAND gate is used to create NOT, AND and OR gate?

(e) Simplify the following Boolean expression using Boolean algebra laws.

$$\overline{AB}(\bar{A} + B)(\bar{B} + B)$$

(f) Simplify using K-map : $y = \sum m(1, 2, 9, 10, 11, 14, 15)$

Q.3 Answer the following (any three)

(15)

(a) Explain Half adder in detail.

(b) Explain 4:1 multiplexer.

(c) Simplify using multiplexer : $y = \sum m(1, 2, 4, 6)$

(d) Explain 2 bit Comparator.

(e) Design 8:1 multiplexer using 4:1 multiplexer.

(f) Explain Full adder in detail.

Q.4 Answer the following (any three)

- (a) Explain R-S flip flop with circuit diagram and truth table.
- (b) Explain D flip flop in detail.
- (c) Solve using K map : $y = \sum m(0, 2, 5, 6, 7, 8, 10, 13, 15)$.
- (d) Draw Half adder using multiplexer.
- (e) Draw Half subtractor using multiplexer.
- (f) Draw 1:16 Demultiplexer using 1:4 Demultiplexer.

(15)

Q.5 Answer the following (any three)

- (a) Explain 3 bit Asynchronous up counter.
- (b) Design MOD 10 counter.
- (c) Explain ALU (IC 74181) in detail.
- (d) Design MOD 12 counter.
- (e) Explain significance of preset and clear input with respect to D Flip flop.
- (f) Explain serial in serial out shift register.

(15)

---X---