

# FYBSC CS/SEM I/REG/Digital System and Architecture

Time: 1 hr.

Marks:30

- Note:
1. All questions are compulsory.
  2. Draw neat diagrams wherever necessary.
  3. Figures to the right indicate full marks.

---

**Q.1** Answer the following. (Any TWO) [10]

- (a) Describe 4:1 multiplexer.
- (b) Write a note on full adder.
- (c) Solve using K map:  $y = \sum m(1,5,6,7,11,12,13,15)$
- (d) Draw AND, OR, NOT and NOR gates using NAND gate.

**Q.2** Answer the following. (Any TWO) [10]

- (a) Find the page Hit and Page miss for the following string using FIFO & LRU page replacement policies considering a frame size three.  
2, 3, 3, 1, 5, 2, 4, 5, 3, 2, 5, 2
- (b) Explain flag register of microprocessor with respect to either 8085 or 8086.
- (c) What is addressing mode? Explain any two in detail.
- (d) Explain what is Instruction cycle. (diagram is mandatory)

**Q.3** Answer the following. (Any TWO) [10]

- (a) Explain half adder with rules, truth table, description and circuit diagram,
- (b) Draw and explain R-S flip flop.
- (c) Explain any three Arithmetic instructions.
- (d) Draw architecture of Microprocessor (Take reference of 8085).

---X---X---