

NEP - Semester End Examination – October 2025

Program: F.Y.BSc.CS	SEM I	Course: Digital System and Architecture
Program Code: UGCS02		Course Code: NUCS101

Duration: 1 Hour Max. Marks: 30

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Draw neat diagrams wherever necessary.

Q. 1	Attempt any TWO of the following.	[10]	Course Outcome	Knowledge Level
(a)	Justify why NAND is called a universal gate by evaluating its ability to implement other logic gates.		CO1	L5
(b)	Explain a Half adder with rules, truth table, description, and circuit diagram.		CO2	L2
(c)	Design and draw the circuit of a D flip-flop and explain its working.		CO4	L6
(d)	Construct 1:4 Demultiplexer (only circuit).		CO3	L1
Q. 2	Attempt any TWO of the following.	[10]	Course Outcome	Knowledge Level
(a)	List and explain any two instructions of data transfer group.		CO1	L1
(b)	Explain the flag register of a microprocessor with reference to either 8085 or 8086.		CO3	L2
(c)	Explain addressing modes and illustrate any two with examples.		CO2	L3
(d)	Construct and explain the architecture of a microprocessor (reference: 8085).		CO4	L6
Q. 3	Attempt any TWO of the following.	[10]	Course Outcome	Knowledge Level
(a)	Differentiate between ADD and ADI & SUB and SUI instructions.		CO1	L1
(b)	Solve the Boolean function $y = \sum m (1, 2, 3, 5, 6, 7, 11, 12, 13, 15)$ using K-map simplification.		CO2	L3
(c)	Calculate the number of page hits and page misses for the given reference string using FIFO & LRU page replacement policies (frame size = 3) 2,3,2,1,5,2,4,5,3,2,5,2		CO4	L3
(d)	Draw Half adder using multiplexer.		CO3	L2

-- X -- X --